

## Three-Phase Grid-Tied Inverter with SRF-PLL Control

This Simulink model implements a Three-Phase Voltage Source Inverter (VSI) tied to a grid/load, utilizing Synchronous Reference Frame (SRF) theory for high-performance current control and grid synchronization.

### System Architecture

The model is divided into two primary sections: the Power Stage (top) and the Control Strategy (bottom).

#### 1. Power Stage

- DC Source: A constant DC voltage input.
- Three-Phase Inverter: A universal bridge controlled by six PWM signals.
- LCL Filter: Inductive-Capacitive-Inductive filtering to suppress high-frequency switching harmonics before reaching the grid.
- Three-Phase Load/Grid: Represented by the AC voltage source and impedance blocks on the far right.
- Measurements: Voltage ( $V_{abc}$ ) and current ( $I_{abc}$ ) sensors provide feedback to the control loops via Go-To/From tags.

#### 2. Control Strategy (Lower Section)

The control logic is implemented in the dq rotating reference frame to simplify the AC signals into DC-like quantities.

- Synchronous Reference Frame PLL (SRF-PLL): \* Uses Clarke ( $\alpha/\beta$ ) and Park (dq) transformations on the grid voltage.
  - A PI controller forces the q-axis voltage to zero, effectively locking the phase angle ( $\Phi$ ) to the grid.
- Current Control Loop:
  - Inner Loop: Separate PI controllers for  $I_d$  (active power/current) and  $I_q$  (reactive power/current).

- Decoupling/Feedforward: Includes cross-coupling terms and grid voltage feedforward to improve dynamic response.
- PWM Generation: \* The resulting control signals are transformed back to the abc frame.
  - A PWM generator converts these signals into the 6 switching pulses (PWM1 through PWM6) for the inverter IGBTs.

### Key Components & Parameters

Component	Description
PowerGui	Set to Discrete mode with a sample time of $1 \times 10^{-6}$
Clarke/Park Transformation	Convert abc to $\alpha\beta$ to dq
PI Controllers	Regulate $I_d$ , $I_q$ and the PLL phase error.
Scope	Monitors real-time output voltage and current for stability analysis.

### How to Use

1. Initialization: Ensure the powergui block is present and set to the desired simulation type (Discrete is recommended for power electronics).
2. Configuration: \* Open the PI controller blocks to tune the Proportional ( $K_p$ ) and Integral ( $K_i$ ) gains.
  - Set the DC link voltage and grid voltage/frequency to match your specific application.
3. Simulation: \* Run the simulation.
  - Open the Scope to observe the sinusoidal output current and its alignment with the grid voltage.
  - Verify that the dq currents track their reference values (1 for  $I_d$  and 200 for  $I_q$  in the current configuration).

## Expected Results

Upon a successful run, the inverter should demonstrate:

- Synchronization: The PLL should converge quickly, providing a stable  $\omega_t$  signal.
- Current Tracking: The measured  $I_d$  and  $I_q$  should reach their respective setpoints with minimal steady-state error.
- Low THD: The LCL filter should ensure the output current waveforms are smooth sinusoids.